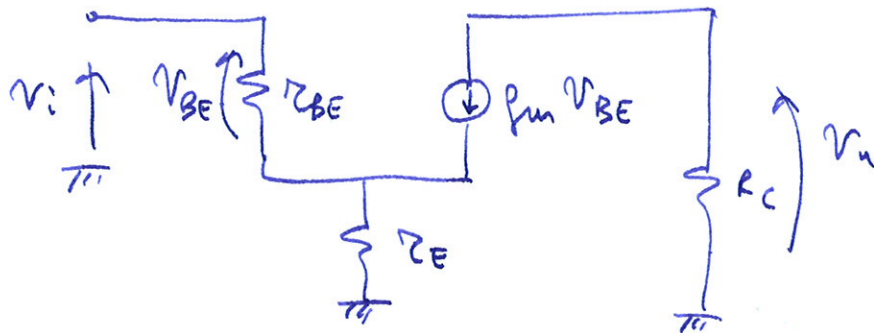


$$1) I_{CO} = \frac{V_{CC} - V_{US}}{R_C} = \frac{3.5 - 2}{750} = 2 \text{ mA} \Rightarrow I_{EO} = 2.04 \text{ mA}$$

La resistenza differenziale del bipolo non lineare è quindi:


$$r_E = R_0 + 3\alpha I_{EO}^2 = 46.2 \Omega$$



$$r_{BE} = \frac{V_T \beta_F}{I_{CO}} = 650 \Omega$$

$$g_m = \frac{I_{CO}}{V_T} = 76.9 \text{ mS}$$
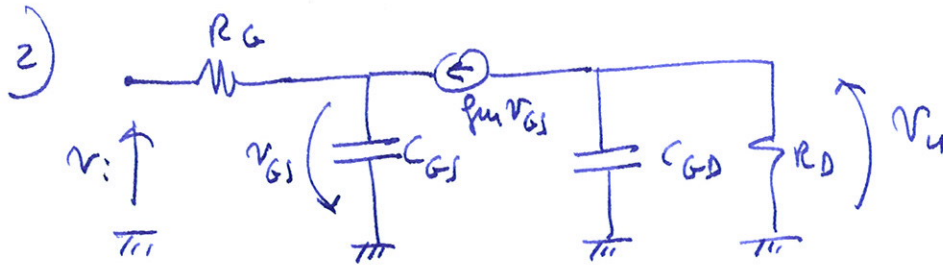
$$\begin{cases} v_u = -g_m v_{BE} R_C \\ v_i = v_{BE} + r_E (g_m + \frac{1}{r_{BE}}) v_{BE} \end{cases} \Rightarrow \frac{v_u}{v_i} = \frac{-g_m R_C}{1 + r_E (g_m + \frac{1}{r_{BE}})} = -12.5$$



$$\begin{cases} v_u = -g_m v_{GS} \cdot \frac{R_D / sC_{GD}}{R_D + \frac{1}{sC_{GD}}} = -\frac{g_m R_D}{1 + sC_{GD} R_D} \cdot v_{GS} \\ \frac{v_i + v_{GS}}{R_G} = -g_m v_{GS} - sC_{GS} v_{GS} \end{cases}$$

$$\Rightarrow \frac{v_u}{v_i} = \frac{g_m R_D}{(1 + sC_{GD} R_D)(1 + R_G g_m + R_G sC_{GS})}$$

$$f_{p1} = \frac{1}{2\pi} \cdot \frac{1}{R_D C_{GD}} = 1.89 \text{ GHz}$$

$$f_{p2} = \frac{1 + R_G g_m}{2\pi R_G C_{GS}} = 63.7 \text{ GHz}$$

$$3) \begin{cases} V^+ = \frac{R_4}{R_4 + R_3 + \frac{1}{sC}} V_u = \frac{sCR_4}{1 + sC(R_3 + R_4)} \cdot V_u \\ V^- = V_i - \frac{V_i - V_u}{R_1 + R_2} \cdot R_1 \\ V_d = V^+ - V^- = \frac{V_u}{A_d} \end{cases}$$

$$\Rightarrow \frac{sCR_4}{1 + sC(R_3 + R_4)} \cdot V_u - \frac{R_2}{R_1 + R_2} \cdot V_i - \frac{R_1}{R_1 + R_2} \cdot V_u = \frac{V_u}{A_d}$$

$$\Rightarrow V_u \left(1 + \frac{R_1 A_d}{R_1 + R_2} - \frac{sCR_4 A_d}{1 + sC(R_3 + R_4)} \right) = -V_i \frac{R_2 A_d}{R_1 + R_2}$$

$$\Rightarrow \frac{V_u}{V_i} = - \frac{R_2 A_d (1 + sC(R_3 + R_4))}{(R_1 + R_2)(1 + sC(R_3 + R_4)) + R_1 A_d (1 + sC(R_3 + R_4)) - sCR_4 A_d (R_1 + R_2)}$$

$$\Rightarrow f_z = \frac{1}{2\pi} \cdot \frac{1}{C(R_3 + R_4)} = 15.9 \text{ kHz}$$

$$4) H_d H_2 = \frac{A_0 e^{-j\omega\tau_2}}{1 + j\omega\tau_1} \Rightarrow \begin{cases} |H_d H_2| = \frac{A_0}{\sqrt{1 + (\omega\tau_1)^2}} \\ \arg(H_d H_2) = -\omega\tau_2 - \arctan(\omega\tau_1) \end{cases}$$

Puisque δ et $MA = 20 \text{ dB}$, donc aussi $\arg(H_d H_2) = -\pi$

donc $|H_d H_2| = -20 \text{ dB}$.

Puisque $\omega_f = \frac{1}{\tau_1} = 10 \text{ rad/s}$, si $\arg(H_d H_2) = -20 \text{ dB}$ pour


$$\omega^* = 10^6 \text{ rad/s}.$$

$$\arg(H_d H_2)|_{\omega=\omega^*} = -\omega^*\tau_2 - \arctan(\omega^*\tau_1) = -\pi$$

$$\Rightarrow \tau_2 = \frac{1}{\omega^*} (\pi - \arctan(\omega^*\tau_1)) = 1.57 \mu\text{s}$$

$$5) H_2 = \frac{V^-}{V_u} = \frac{R_3}{R_2 + R_3} \quad ; \quad H_d H_2 = \frac{\frac{A_0 R_3}{R_2 + R_3}}{(1+j\frac{\omega}{\omega_{p1}})(1+j\frac{\omega}{\omega_{p2}})}$$

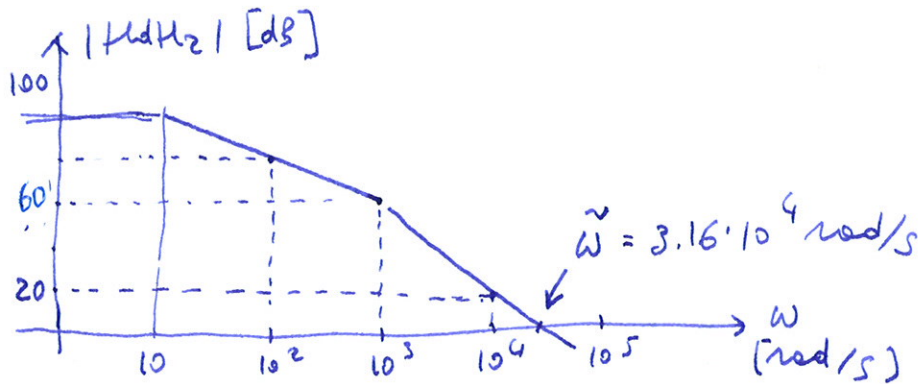
$$\frac{A_0 R_3}{R_2 + R_3} = 10^5 = 100 \text{ dB}$$



$$\arg(H_d H_2) \big|_{\omega=\tilde{\omega}} = -\arctan\left(\frac{\tilde{\omega}}{\omega_{p1}}\right) - \arctan\left(\frac{\tilde{\omega}}{\omega_{p2}}\right) =$$

$$= -89.98^\circ - 88.19^\circ = 178.2^\circ$$

$$\Rightarrow MF = 1.8^\circ$$

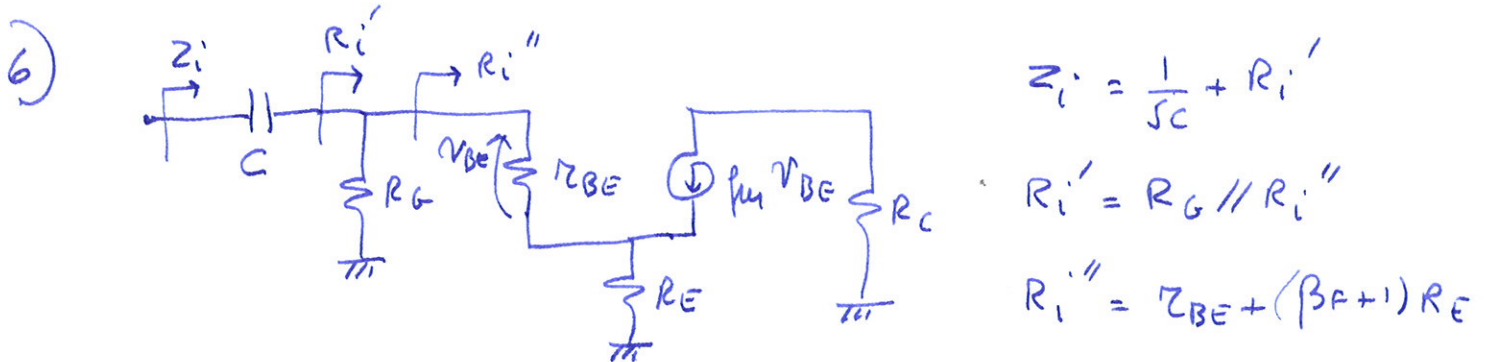

$$I_{B0} + \frac{V_{CC} - (\beta_F I_B R_E + V_{BE})}{R_G} = I_B \Rightarrow I_B = \frac{R_G I_{B0} + V_{CC} - V_{BE}}{R_G + \beta_F R_E} = 14.5 \mu A$$

$$\Rightarrow r_{BE} = 1.79 \text{ k}\Omega$$

$$\Rightarrow R_i'' = 3.61 \text{ k}\Omega \Rightarrow R_i' = 3.58 \text{ k}\Omega$$

$$Z_i = R_i' - \frac{j}{\omega C} \Rightarrow |Z_i| = \sqrt{(R_i')^2 + \left(\frac{1}{(2\pi f C)}\right)^2} = 3.73 \text{ k}\Omega$$

$$7) \quad \frac{1}{2} (\mu_p C_{ox}) \left(\frac{W}{L} \right)_1 (V_{SG1} + V_{TP})^2 = \frac{V_{SS} - V_{SG1}}{R}$$

$$\Rightarrow 6 \cdot 10^{-4} \cdot V_{SG1}^2 - 1.2 \cdot 10^{-3} \cdot V_{SG1} + \cancel{6 \cdot 10^{-4}} = \cancel{6 \cdot 10^{-4}} - 2 \cdot 10^{-4} \cdot V_{SG1}$$

$$\Rightarrow V_{SG1} (6 \cdot 10^{-4} \cdot V_{SG1} - 10^{-3}) = 0$$

$$\Rightarrow V_{SG1} = \begin{cases} 0 \text{ V} : \text{solution de l'équation} \\ 1.67 \text{ V} : \text{solution acceptable} \end{cases}$$

$$\Rightarrow I_{D1} = 266 \mu\text{A} \Rightarrow I_{D2} = \frac{1}{4} I_{D1} = 66.5 \mu\text{A}$$

$$\Rightarrow I_{D3} = \frac{1}{2} (\mu_n C_{ox}) \left(\frac{W}{L} \right)_3 (V_{G0} - V_{TN})^2 (1 + \lambda_3 \cdot V_0) = I_{D2}$$

$$\Rightarrow V_0 = \frac{1}{\lambda_3} \left(\frac{I_{D2}}{\frac{1}{2} (\mu_n C_{ox}) \left(\frac{W}{L} \right)_3 (V_{G0} - V_{TN})^2} - 1 \right) = 1.93 \text{ V}$$

$$8) \quad V_0 = R_0 (I_{E2} - I_{C1})$$

$$I_{C1} = \beta_F \cdot I_{B1} = \beta_F \cdot \frac{V_{B1} - V_{\gamma}}{R_{B1}} = 2.5 \text{ mA}$$

$$I_{E2} = (\beta_F + 1) I_{B2} = (\beta_F + 1) \frac{V_{B2} - V_{\gamma} - V_0}{R_{B2}}$$

$$\Rightarrow V_0 = R_0 \left((\beta_F + 1) \frac{V_{B2} - V_{\gamma} - V_0}{R_{B2}} - \beta_F \cdot \frac{V_{B1} - V_{\gamma}}{R_{B1}} \right)$$

$$\Rightarrow V_0 \left(1 + (\beta_F + 1) \frac{R_0}{R_{B2}} \right) = R_0 \left((\beta_F + 1) \frac{V_{B2} - V_{\gamma}}{R_{B2}} - \beta_F \frac{V_{B1} - V_{\gamma}}{R_{B1}} \right)$$

$$\Rightarrow V_0 = 1.39 \text{ V}$$