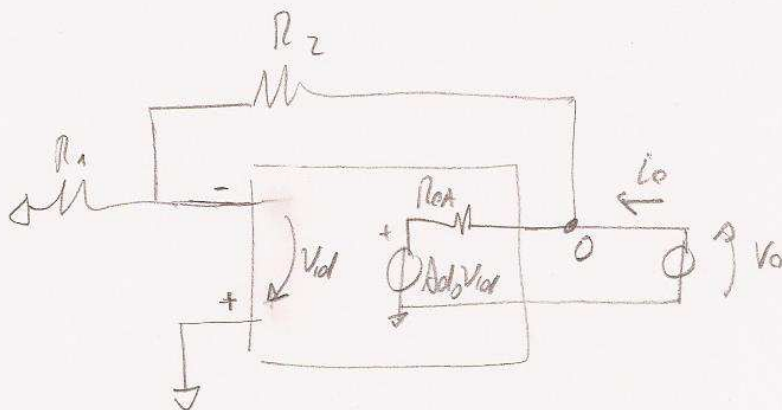


1)



BILANCIO \bar{I} AL NODO O


$$I_o = (V_o - A_{d0} V_{id}) G_{OA} + V_o G_{R2}$$

$$V_{id} s - V_o \cdot \frac{R_1}{R_1 + R_2} = -V_o U_r$$

$$G_{R2} = \frac{1}{R_1 + R_2}$$

$$U_r = \frac{R_1}{R_1 + R_2}$$
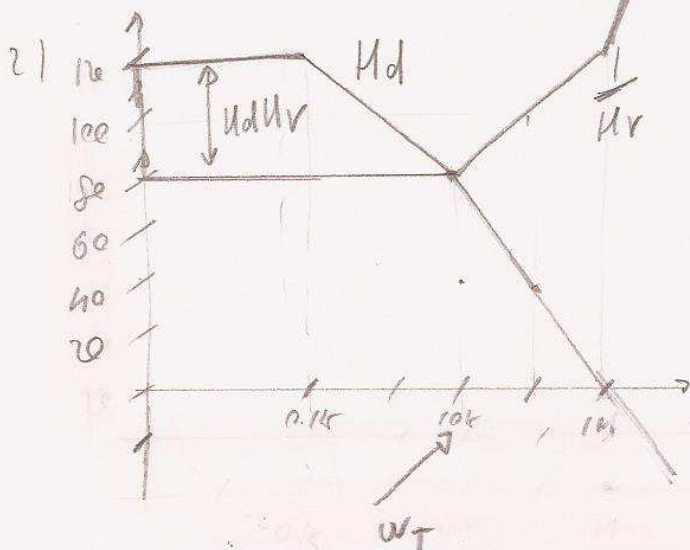
$$R_o = \frac{V_o}{I_o} = \frac{1}{[1 + A_{d0} U_r] \frac{1}{R_{OA}} + \frac{1}{R_1 + R_2}} \approx 240 \Omega$$



$$G_{OA} U_{r0} = -80 \text{ dB}$$

$$|U_d U_r|_{\omega = 10 \text{ K}} = 0 \text{ dB}$$

$$\angle U_d U_r|_{\omega = 10 \text{ K}} = -135^\circ$$

$$\Rightarrow PM_s = 45^\circ$$

$$U_{r0} = -80 \text{ dB}$$


3)

$$V_{DS1} = V_{GS1} - I_{B1} R_1 \quad I_{B1} R_1 < V_{TH} \Rightarrow M1 \text{ SAT!}$$

$$V_{DS1} = V_{DS2}, \quad \lambda \approx 0 \text{ for } M1 \text{ e } M2 \Rightarrow$$

$$\Rightarrow I_{D2} = I_{D1} \cdot \frac{(W/L)_2}{(W/L)_1} = I_{D1} = I_{B1}$$

$$I_O = I_{D2} - I_{B2} = 138 \mu A$$

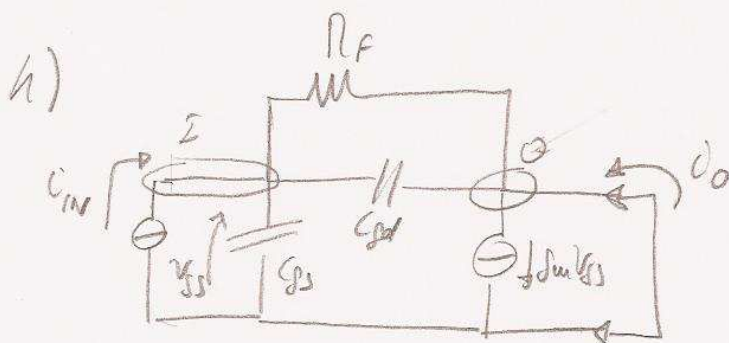

$$I: \quad C_{IN} s \quad v_g1 [s(C_{gs} + C_{gd}) + G_F]$$

$$O: \quad C_O s \quad v_o = g_m v_g1 - v_o (s C_{gd} + G_F)$$

$$G_F = \frac{1}{R_F}$$

$$A_V = \frac{C_O}{C_{IN}} = \frac{(g_m - G_F) - s C_{gd}}{G_F + s(C_{gd} + C_{gs})}$$

$$C_X = C_{gd} + C_{gs}$$

$$|A_V(\omega_f)|_{s=j\omega} \rightarrow \omega_f^2 (C_X^2 - C_{gd}^2) = g_m^2$$

$$\rightarrow (I_m - I_F)^2 + \omega_T^2 I_d^2 = I_F^2 + C_x^2 \omega_T^2$$

$$\Rightarrow I_m^2 - 2 I_m I_F - \omega_T^2 (C_x^2 - I_d^2) = 0$$

1 sola soluzione ammissibile ($I_m > 0$)

$$I_m = 143 \mu$$

$$I_m = \sqrt{2 I_F' \frac{V_T}{L} I_B} \rightarrow I_B = 85.2 \mu A$$

5)

BILANCIO AL NODO B (BASE)

$$I_X = I_{R_B} + I_B$$

MAGLIA

$$I_E R_E + V_d + R_B (I_B + I_X) = V_{DD}$$

$$I_C = \frac{V_{DD} - V_d - R_B I_X}{(B+1) R_E + R_B} \cdot \beta = 336 \mu A$$

6)

Sovrapposizione degli effetti

a) $V_{i1} = 0, I_{B1} = 0$

$$V_{o1} = - \left(\frac{\beta R_1}{r_i} \right) V_{i1} = -5 V_{i1}$$

b) $V_{i1} = 0, I_{B1} = 0$


$$V_{o2} = V_{o1} \left(\frac{\beta R_1}{R_1} \right) + V_{i2} = 10 \cdot V_{i2}$$

c) $V_{i1} = 0, V_{i2} = 0$

$$V_{o2} = \beta R_1 \cdot I_{B1}$$

$$V_{o1} + V_{o2} + V_{o3} + V_{o4} = -100mV$$

71

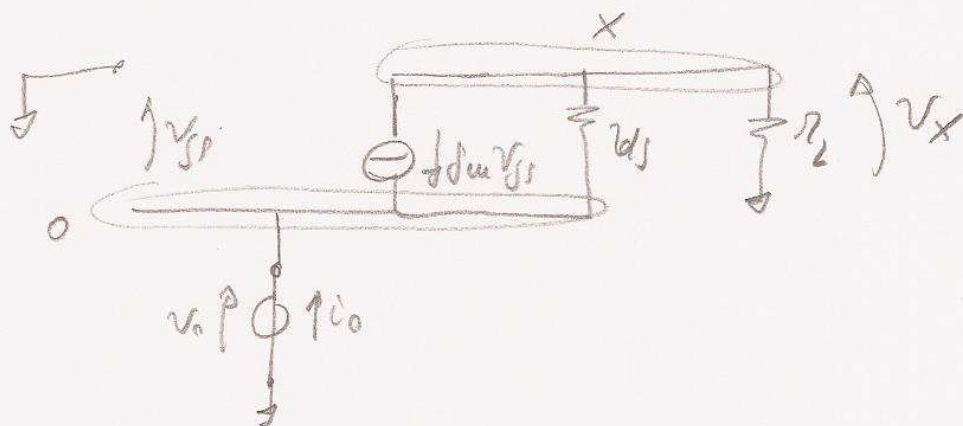

$$g_L \approx \frac{1}{r_L}$$

$$0: C_0 \approx g_m V_0 + (V_0 - V_s) g_{ds}$$

$$(V_{gs} - V_0)$$

$$s: V_s g_L - g_m V_0 + g_{ds} (V_s - V_0) = 0$$

$$R_{eq} \approx \frac{V_0}{C_0} \bigg|_{V_{in} = 0} = \frac{g_L + g_{ds}}{g_m g_L + g_{ds} g_L} = \frac{r_{ds} + r_L}{r_{ds} g_m + 1} \approx 5.4 \text{ k}\Omega$$

