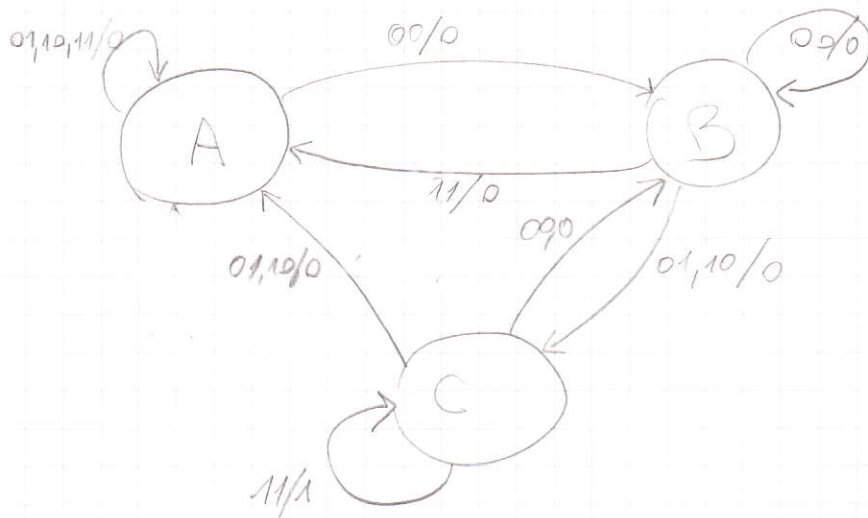


Esercizio 2

Progettare una rete sequenziale sincrona che scriva l'andamento di 2 segnali in ingresso x, y . L'uscita z avrà valore 1 quando si verifica 1 delle condizioni $(00, 01, 11)$ o $(00, 10, 11)$. z rimane inalterato fino a che rimane config. iniziale (11) .

FF-JK



automa

		00	01	11	10
00 $\Rightarrow$ A		B, 0	A, 0	A, 0	A, 0
01 $\Rightarrow$ B		B, 0	C, 0	A, 0	C, 0
10 $\Rightarrow$ C		B, 0	A, 0	C, 1	A, 0

$\frac{xy}{FF_2}$	00	01	11	10
00	01, 0	00, 0	00, 0	00, 0
01	01, 0	10, 0	00, 0	10, 0
10	01, 0	00, 0	01, 1	00, 0

tab. transizioni

come decade	funzione di CK	J	K	uscita Q_{n+1}
0	-	-	-	Q_n
1	0	0	0	Q_n
1	0	0	1	0
1	1	0	0	1
1	1	1	1	Q_n^*

presente Q_n	futuro Q_{n+1}	J	K
0 $\Rightarrow$ 0	0	0	-
0 $\Rightarrow$ 1	1	1	-
1 $\Rightarrow$ 0	0	-	1
1 $\Rightarrow$ 1	1	-	0

x	y	F ₁	F ₂	F ₁₊	F ₂₊	J ₁	K ₁	J ₂	K ₂	z
0	0	0	0	0	1	0	-	1	-	0
0	0	0	1	0	1	0	-	-	0	0
0	0	1	0	0	1	-	1	1	-	0
0	0	1	1	-	-	-	-	-	-	1
0	1	0	0	0	0	0	-	0	-	0
0	1	0	1	1	0	1	-	-	1	0
0	1	1	0	0	0	-	1	0	-	0
0	1	1	1	-	-	-	-	-	-	1
1	0	0	0	0	0	0	-	0	-	0
1	0	0	1	1	0	1	-	-	1	0
1	0	1	0	0	0	1	1	0	-	0
1	0	1	1	0	0	1	0	1	-	0
1	1	0	0	0	0	0	-	0	-	0
1	1	0	1	1	0	1	-	-	1	0
1	1	1	0	0	0	0	1	0	-	0
1	1	1	1	1	1	1	1	1	1	1

tabella verità

J1

$F_1 F_2 \backslash xy$	00	01	11	10
00	0	0	0	0
01	0	1	0	1
11	1	1	1	1
10	1	1	1	1

Soluzioni

$$J_1 = F_2 \bar{x}y \oplus F_2 x \bar{y}$$

AND OR

K1

$F_1 F_2 \backslash xy$	00	01	11	10
00	-	-	1	-
01	-	-	1	-
11	-	-	1	-
10	1	1	0	1

$$K_1 = \bar{x} + \bar{y}$$

OR

J2

$F_1 F_2 \backslash xy$	00	01	11	10
00	1	0	0	0
01	1	1	1	1
11	1	1	1	1
10	1	0	0	0

$$J_2 = \bar{x}y$$

AND

K2

$F_1 F_2 \backslash xy$	00	01	11	10
00	-	-	-	-
01	0	1	1	1
11	1	1	1	1
10	1	1	1	1

$$K_2 = x + y$$

OR


raccoltim. maggior. poss.

Z

$F_1 F_2 \backslash xy$	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	0	0	1	0

$$Z = F_1 xy$$

AND

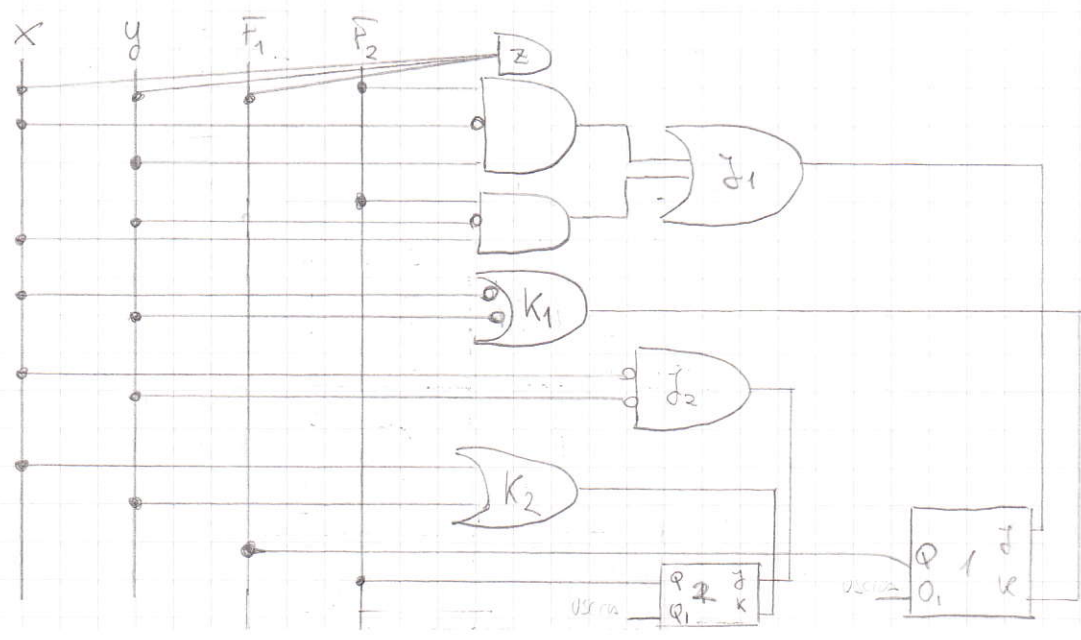

simplify:

$$F(x, y, z) = \bar{x}y\bar{z} + \bar{x}yz + x\bar{y}\bar{z} + x\bar{y}z$$

$\begin{matrix} x/y \\ z \end{matrix}$	00	01	11	10
0	0	1	0	1
1	0	1	0	1

 $\bar{x}y$ $x\bar{y}$

$$= \bar{x}y + x\bar{y} = x \oplus y$$

simplify:

let D has value 0 or 1

$$F(A, B, C, D) = \bar{A}\bar{B}\bar{C} + \bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C}\bar{D}$$

$\begin{matrix} C/D \\ AB \end{matrix}$	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	0	0	0	0
10	1	1	0	1

 $\bar{B}\bar{C}$

$$= \bar{A}\bar{C}\bar{D} + \bar{B}\bar{C} + \bar{B}\bar{D}$$

simplify:

$$F(x, y, z) = x\bar{y}\bar{z} + x\bar{y}z + x\bar{y}z + x\bar{y}z + \bar{x}y\bar{z} + \bar{x}yz$$

in 1st case (particolarmente faticoso) facciamo senza mappe

$$= x\bar{z}(\underbrace{\bar{y}+y}_1) + xz(\underbrace{\bar{y}+y}_1) + \bar{x}y(\underbrace{\bar{z}+z}_1) = x\bar{z} + xz + \bar{x}y =$$

$$= x(\bar{z}+z) + \bar{x}y = x + \bar{x}y$$

prop. distribut. $= (x + \bar{x})(x + y) = x + y$



Feb. 2004

$$DB \oplus (DA + AB) = DAB + \overline{DAB}$$

AB	00	01	11	10
D	0	0	1	0
0	0	0	1	0
1	1	0	0	0


DA DB

A	B	A ⊕ B
0	0	0
0	1	1
1	0	1
1	1	0

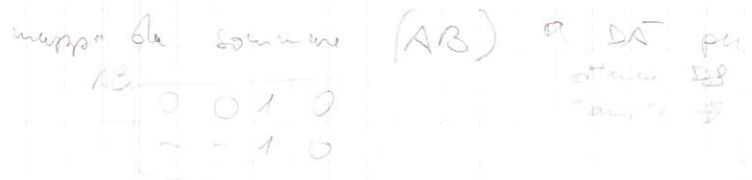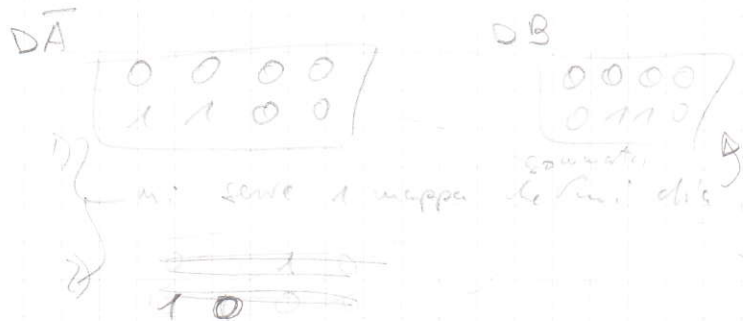

RETE SEQUENZIALE SINCRONA

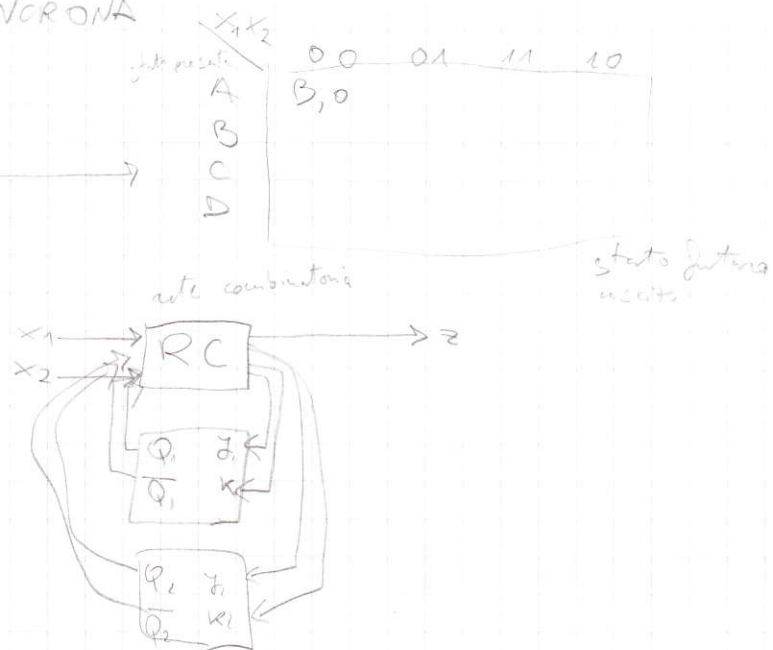- 1) forme d'onda
- 2) automa (ASF)
- 3) tabella di transizione
- 4) modello di Huffman




- 5) tabella verità

es

2.5.16



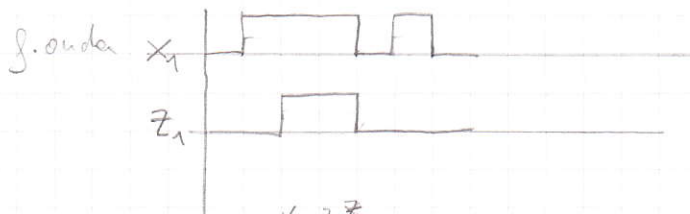- a) $x_1 = x_2 = 1$ MAI gli ingressi non possono salire a 1 entrambi
 b) $z_1 = 1$ se x_1 resta 1 per almeno 2 intervalli consecutivi
 $z_2 = 1$ se x_2 resta 1 per almeno 2 intervalli consecutivi



automa


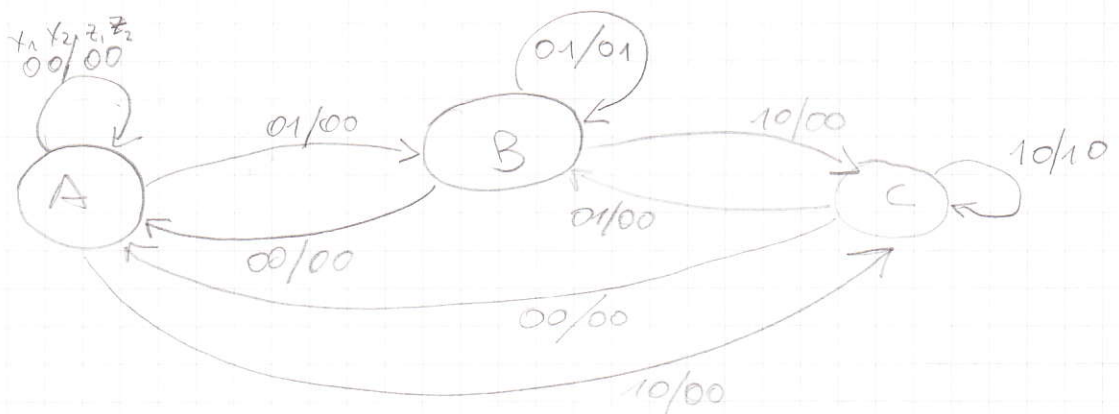


tabella transizione

$x_1 x_2$		$y_1 y_2$				$Q_n \Rightarrow Q_{n+1}$		J	K		
		00	01	10	11	0	1	0	1	z_1	z_2
A = 00		A, 00	B, 00	C, 00	/	0	0	0	1	-	-
B = 01		A, 00	B, 01	C, 00	/	1	0	-	-	1	-
C = 10		A, 00	B, 00	C, 10	/	1	1	-	-	0	-
11		/	/	/	/	0	-	-	-	-	-

x_1	x_2	y_1	y_2	y_{1+}	y_{2+}	J_1	K_1	J_2	K_2	z_1	z_2
0	0	0	0	0	0	0	-	0	-	0	0
0	0	0	1	0	0	0	-	-	1	0	0
0	0	1	0	0	0	-	1	0	-	0	0
0	0	1	1	-	-	-	-	-	-	1	1
0	1	0	0	0	1	0	-	1	-	0	0
0	1	0	1	0	1	0	-	-	0	0	1
0	1	1	0	0	1	-	1	1	-	0	0
0	1	1	1	-	-	-	-	-	-	-	-
1	0	0	0	1	0	1	-	0	-	0	0
1	0	0	1	1	0	1	-	-	1	0	0
1	0	1	0	1	0	-	0	0	-	1	0
1	0	1	1	-	-	-	-	-	-	-	-
1	1	0	0	-	-	-	-	-	-	-	-
1	1	0	1	-	-	-	-	-	-	-	-
1	1	1	0	-	-	-	-	-	-	-	-
1	1	1	1	-	-	-	-	-	-	-	-

modello di Huffman

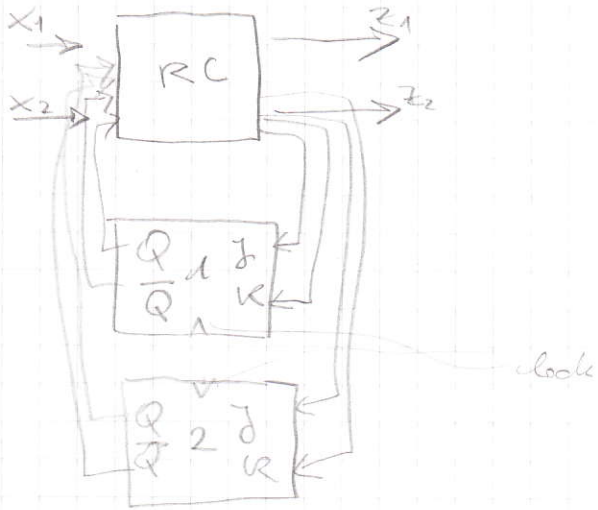

J_1

$x_1 x_2$	00	01	11	10
$y_1 y_2$	00	00	11	11
01	0	0	1	1
11	1	1	1	1
10	1	1	1	1

$J_1 = x_1$

K_1

$x_1 x_2$	00	01	11	10
$y_1 y_2$	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	0

$K_1 = \overline{x_1}$

J_2

$x_1 x_2$	00	01	11	10
$y_1 y_2$	00	01	11	10
00	0	1	1	0
01	1	1	1	1
11	1	1	1	1
10	0	1	1	0

$J_2 = x_2$

K_2


$x_1 x_2$	00	01	11	10
$y_1 y_2$	00	01	11	10
00	1	1	1	1
01	1	0	1	1
11	1	1	1	1
10	1	1	1	1

$K_2 = \overline{x_2}$

z_1

$x_1 x_2$ $y_1 y_2$	00	01	11	10
00	0	0	-	0
01	0	0	-	0
11	-	-	-	-
10	0	0	-	1


$z_1 = x_1 y_1$

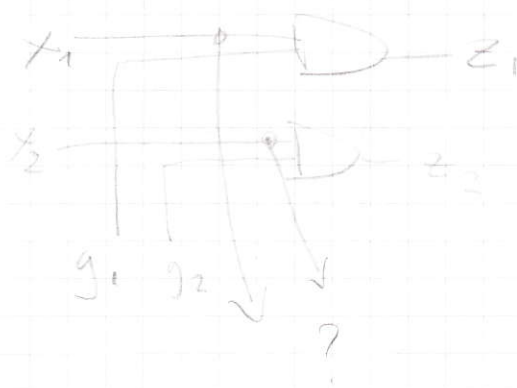

z_2

$x_1 x_2$ $y_1 y_2$	00	01	11	10
00	0	0	-	0
01	0	1	-	0
11	-	-	-	-
10	0	0	-	0

$z_2 = x_2 y_2$

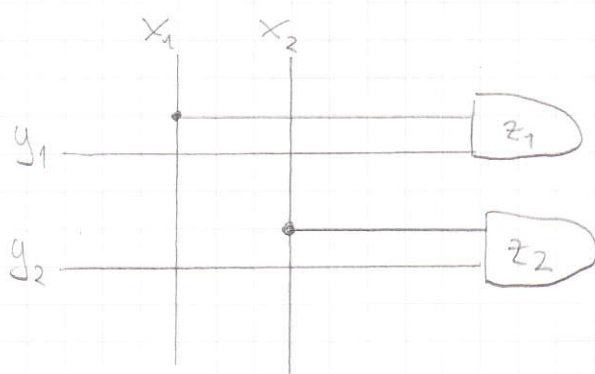

somme di prodotti
 SP $\rightarrow$ NAND
 PS $\rightarrow$ NOR
 prodotti di somme

$$\begin{aligned}
 z_{SP} &= (x_1 x_2) + (x_3 x_4) = \overline{(x_1 x_2) + (x_3 x_4)} = \\
 &= \overline{(x_1 x_2)} \cdot \overline{(x_3 x_4)} = \overline{(x_1 \uparrow x_2)} \cdot \overline{(x_3 \uparrow x_4)} = \\
 &= (x_1 \uparrow x_2) \uparrow (x_3 \uparrow x_4)
 \end{aligned}$$

esame 29 aprile 2004/a


$$A+B=1 \quad AB=0$$

1)

$$AC + \bar{A}B + BC = B + C$$

$$\begin{aligned} c(A+B) + \bar{A}B &= c + \bar{A}B + \overbrace{AB}^0 = c + B(\bar{A}+A) = \\ &= c + B \end{aligned}$$

3)

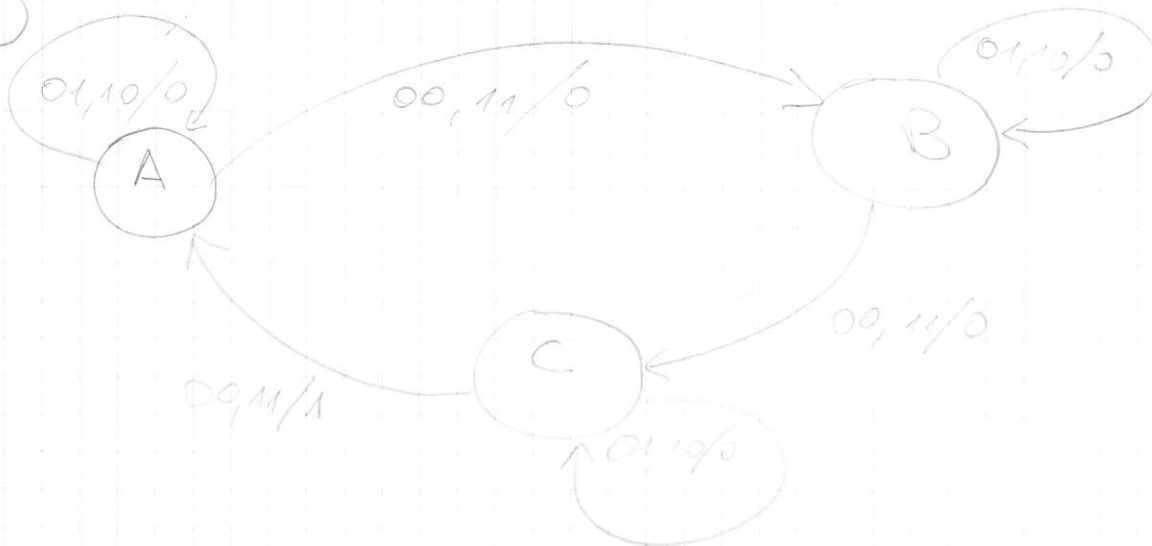

x_1, x_2	00	01	10	11
00 - A	B, 0	A, 0	A, 0	B, 0
01 - B	C, 0	B, 0	B, 0	C, 0
10 - C	A, 1	C, 0	C, 0	A, 1

x_1, x_2	00	01	10	11
00	01, 0	00, 0	00, 0	01, 0
01	10, 0	01, 0	01, 0	10, 0
10	00, 1	10, 0	10, 0	00, 1

tabella transizioni

Q_n	Q_{n+1}	J	K
0	0	0	-
0	1	1	-
1	0	-	1
1	1	-	0

x_1	x_2	y_1	y_2	y_{1+}	y_{2+}	f_1	K_1	f_2	K_2	z
0	0	0	0	0	1	0	-	1	-	0
0	0	0	1	1	0	1	-	-	1	0
0	0	1	0	0	0	-	1	0	-	1
0	0	1	1	-	-	-	-	0	-	-
0	1	0	0	0	0	0	-	0	-	0
0	1	0	1	0	1	0	-	0	1	0
0	1	1	0	1	0	1	0	0	-	0
0	1	1	1	-	-	-	-	0	-	1
1	0	0	0	0	0	0	1	0	-	0
1	0	0	1	0	1	0	1	0	-	0
1	0	1	0	1	0	-	0	0	1	0
1	0	1	1	-	-	-	-	-	-	-
1	1	0	0	0	1	0	-	1	-	0
1	1	0	1	1	0	1	-	1	1	0
1	1	1	0	0	0	-	1	0	-	1
1	1	1	1	-	-	-	-	-	-	-

f_1

$x_1 x_2$	00	01	11	10
00	0	0	0	0
01	1	0	0	1
11	-	-	-	-
10	-	-	-	-

$f_1 = \overline{x_2} y_1$

K_1

$x_1 x_2$	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	0	0	1

$K_1 = \overline{x_2}$

f_2

$x_1 x_2$	00	01	11	10
00	1	0	0	1
01	1	1	1	1
11	1	1	1	1
10	0	0	0	0

$f_2 = y_1 \overline{x_2}$

K_2

$x_1 x_2$	00	01	11	10
00	1	1	1	1
01	1	0	0	1
11	1	1	1	1
10	1	0	0	1

$K_2 = \overline{x_2}$

z

$\frac{x_1 x_2}{y_1 y_2}$	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	0	0
10	1	0	0	1

$$z = \overline{x_2} y_1$$

ASSORBIMENTO $X + X \cdot Y = X$

es

$$X + \overline{X} Y = X + Y$$

$$X + X Y + \overline{X} Y = X + Y (\overline{X} + X)$$

X

X + Y

$$\overline{X + \overline{X} Y} \rightarrow \overline{X \cdot \overline{X} Y} \rightarrow \overline{X \cdot (\overline{X} + Y)}$$

DE MORGAN

$$X \cdot (\overline{X} + Y)$$

$\frac{y}{x}$	0	1
0	0	1
1	1	1

KARNAUGH

$$X + Y$$

29 apr 2004/6

1) $D+B=1$ $DB=0$


verifier $BC + \bar{D}B + DC = B + C$


$$C(D+B) + \bar{D}B = C + \bar{D}B = C + \bar{D}B + DB =$$

$$= C + B(\bar{D}+D) = C+B$$

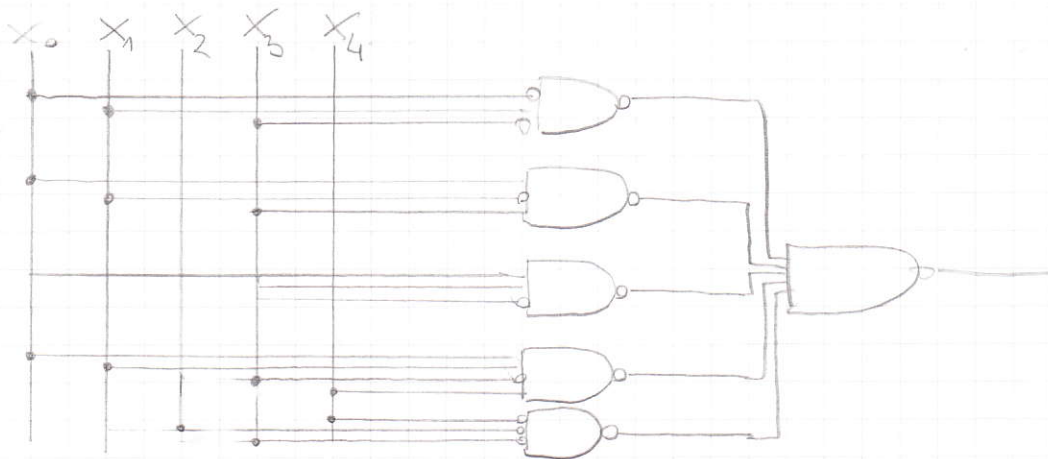5)

$$\bar{x}_0 x_1 \bar{x}_3 + x_0 \bar{x}_1 x_3 + x_0 x_3 \bar{x}_4 + x_0 x_2 \bar{x}_3 x_4 + \bar{x}_2 x_3 x_4$$



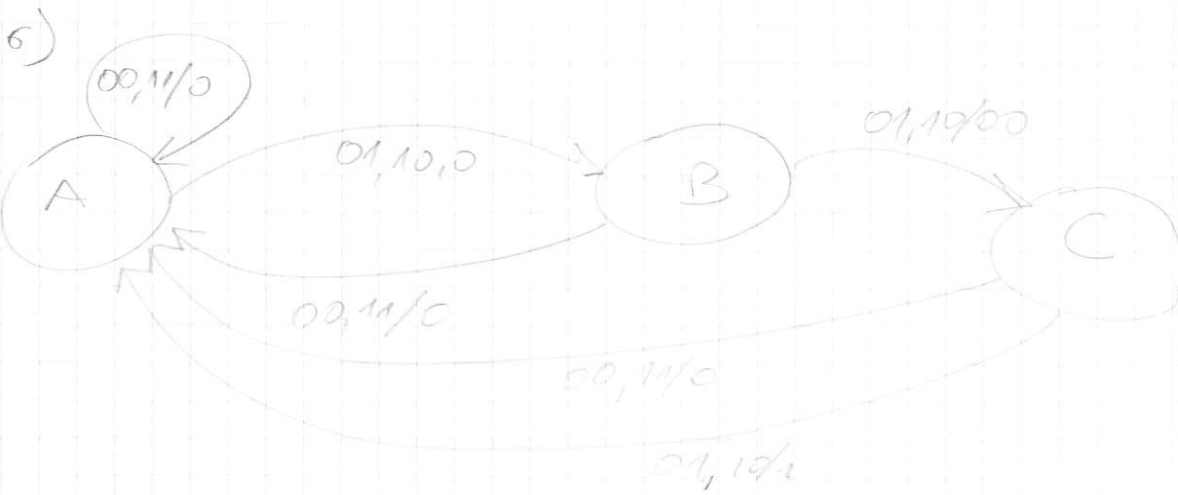

$x_1 x_2$	00	01	10	11
A	A, 0	B, 0	B, 0	A, 0
B	A, 0	C, 0	C, 0	A, 0
C	A, 0	A, 1	A, 1	A, 0

$y_1 y_2$	00	01	10	11
00	00, 0	01, 0	01, 0	00, 0
01	00, 0	10, 0	10, 0	00, 0
10	00, 0	00, 1	00, 1	00, 0

Tab. Transitions:

$Q_n \Rightarrow Q_{n+1}$	J	K
0	0	-
0	1	-
1	-	1
1	-	0

x_1	x_2	y_1	y_2	y_{1+}	y_{2+}	J_1	K_1	J_2	K_2	Z
0	0	0	0	0	0	0	-	0	-	0
0	0	0	1	0	0	0	-	-	1	0
0	0	1	0	0	0	1	1	0	-	0
0	0	1	1	1	1	1	1	0	-	0
0	1	0	0	0	1	0	-	1	-	0
0	1	0	1	1	0	1	-	-	1	0
0	1	1	0	0	0	-	1	0	-	1
0	1	1	1	1	1	-	1	0	-	1
1	0	0	0	0	1	0	-	1	-	0
1	0	0	1	1	0	1	-	-	1	0
1	0	1	0	0	0	-	1	0	-	1
1	0	1	1	1	1	-	1	0	-	1
1	1	0	0	0	0	0	-	0	-	0
1	1	0	1	0	0	0	-	-	1	0
1	1	1	0	0	0	1	1	0	-	0
1	1	1	1	1	1	-	-	-	-	-

f_1

$x_1 x_2$ $y_1 y_2$	00	01	11	10
00	0	0	0	0
01	0	1	0	1
11	1	1	1	1
10	1	1	1	1

$$f_1 = \overline{x_1} x_2 y_2 + x_1 \overline{x_2} y_2$$

K_1

-	-	-	-
-	-	-	-
-	-	-	-
1	1	1	1

f_2

	01	10
00	0	1
01	1	1
11	1	1
10	0	0

$$f_2 = \overline{x_1} x_2 \overline{y_1} + x_1 \overline{x_2} y_1$$


K_2

-	-	-	-
1	1	1	1
-	-	-	-
-	-	-	-

z



	01	10
00	0	0
01	0	0
11	1	1
10	0	0
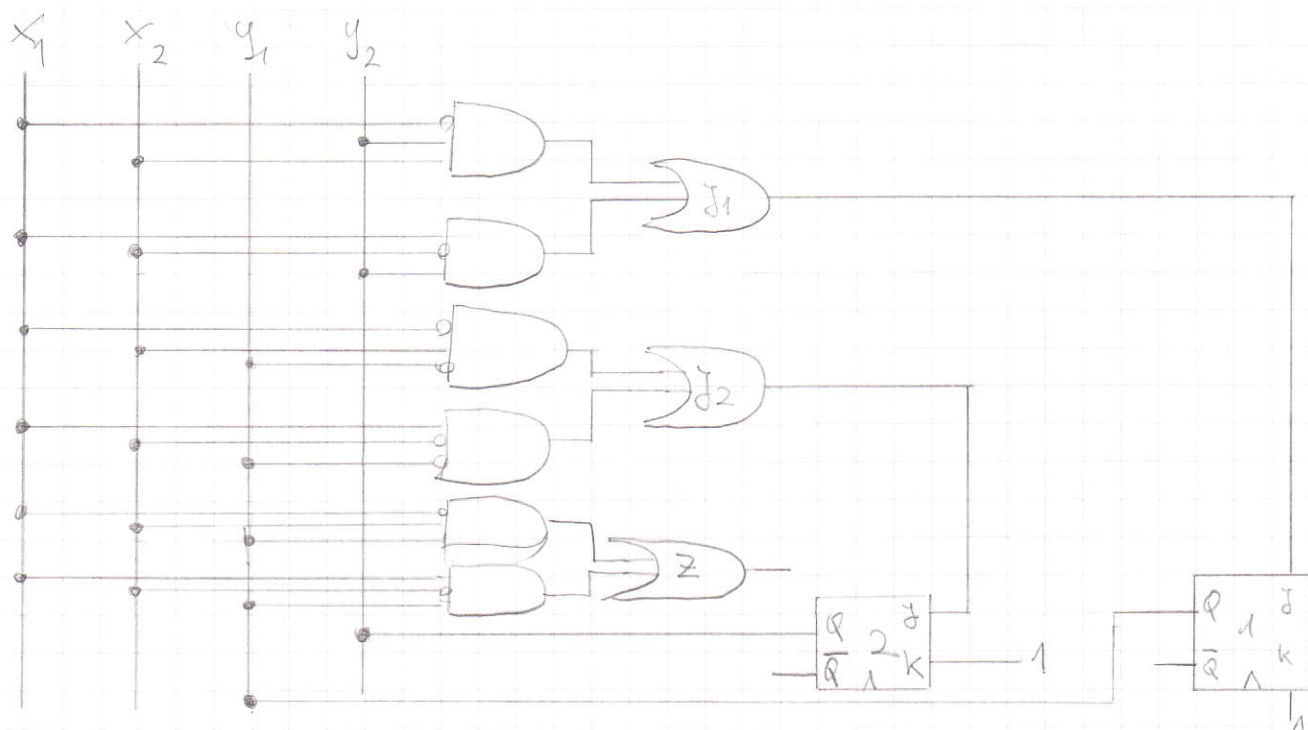
$$z = \overline{x_1} x_2 y_1 + x_1 \overline{x_2} y_1$$





24 giugno 2004

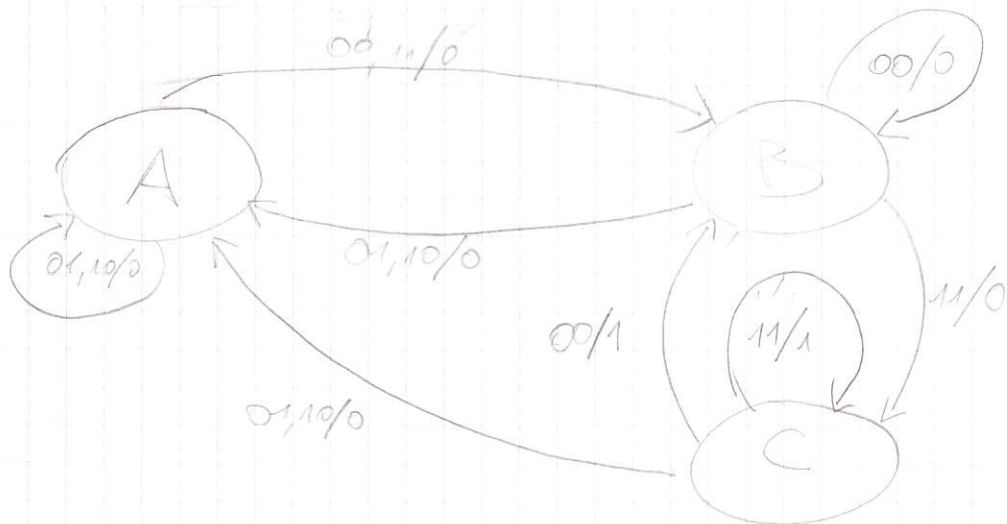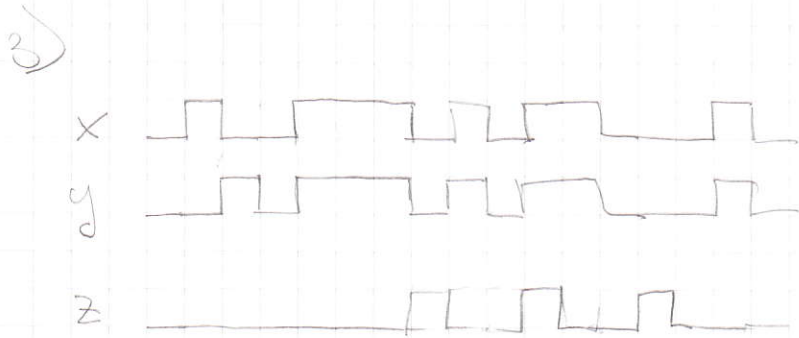2) $\overline{x_0}x_1 + x_1\overline{x_2} + x_0\overline{x_1}x_2\overline{x_4} + x_1x_3\overline{x_4} + x_0x_2\overline{x_3}x_4$



es. 3 NO $x_1 = x_2 = 0$

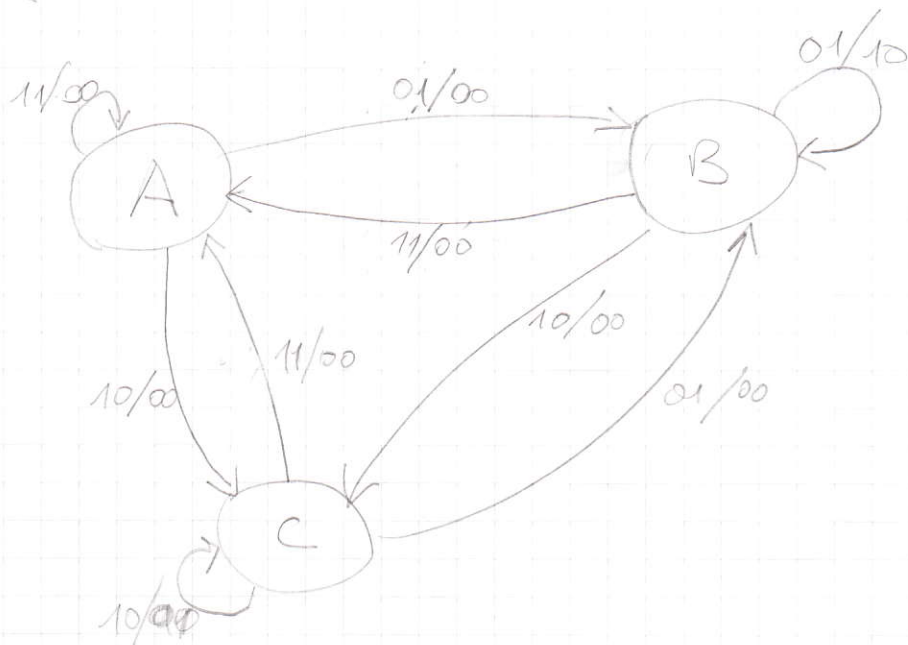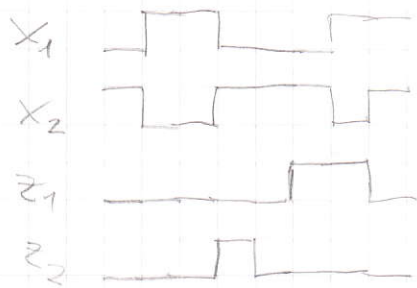

15 luglio 04

semplificazione ^{e implementare} (con soli NOR)

1)

$$A\bar{B}\bar{C} + AC + \bar{A}C\bar{D}$$

$$\begin{pmatrix} AB = \overline{\bar{A} + \bar{B}} \\ \overline{AB} = \bar{A} + \bar{B} \end{pmatrix}$$

$$A\bar{B}\bar{C} + AC(\bar{B} + 1) + \bar{A}C\bar{D}$$

$$A\bar{B}\bar{C} + A\bar{B}C + AC + \bar{A}C\bar{D}$$

$$A\bar{B}(\bar{C} + C) + AC + \bar{A}C\bar{D}$$

$$A\bar{B} + AC + \bar{A}C\bar{D}$$

$$A\bar{B} + AC(\bar{D} + 1) + \bar{A}C\bar{D}$$

$$A\bar{B} + AC\bar{D} + AC + \bar{A}C\bar{D}$$

$$A\bar{B} + AC + C\bar{D}(A + \bar{A})$$

$$\boxed{A\bar{B} + AC + C\bar{D}}$$

con NOR

$$(\bar{A} + B) \cdot (\bar{A} + \bar{C}) \cdot (\bar{C} + D)$$

$$(\bar{A}\bar{A} + \bar{A}B + A\bar{C} + B\bar{C}) \cdot (\bar{C} + D)$$

$$\bar{A}\bar{A}\bar{C} + \bar{A}B\bar{C} + A\bar{C}\bar{C} + B\bar{C}\bar{C} + \bar{A}\bar{A}D + \bar{A}BD + A\bar{C}D + B\bar{C}D$$

$$\bar{A}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{C} + B\bar{C} + \bar{A}D + \bar{A}BD + A\bar{C}D + B\bar{C}D$$

$$\bar{A}\bar{C} + B\bar{C} + \bar{A}D$$

$$\bar{A}\bar{C} + \bar{A}D + B\bar{C} = \overline{(A + C)} + \overline{(A + \bar{D})} + \overline{(\bar{B} + C)}$$

oppure con



mappe Karnaugh

$$\bar{A}\bar{B} + C\bar{D} + AC$$

AB \ CD	00	01	11	10
00	0	0	0	1
01	0	0	0	1
11	0	0	1	1
10	1	1	1	1



$x = 512$

3)

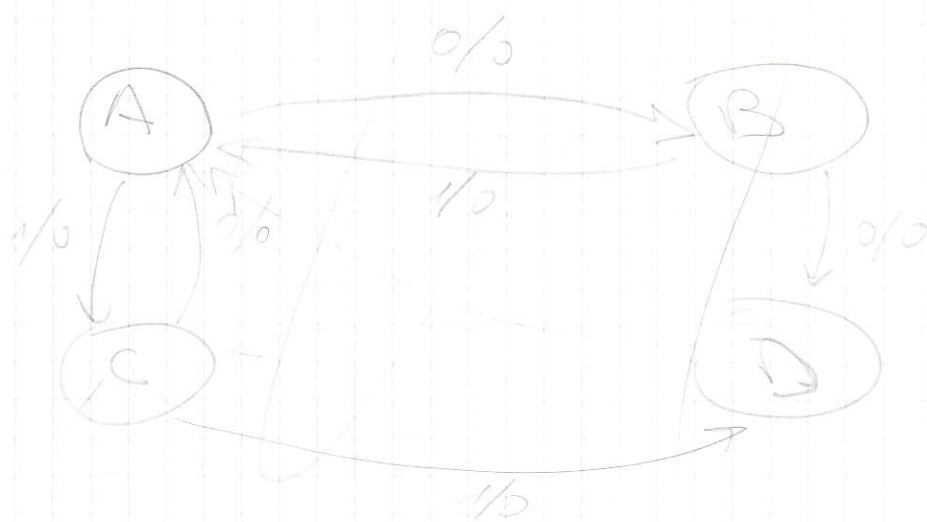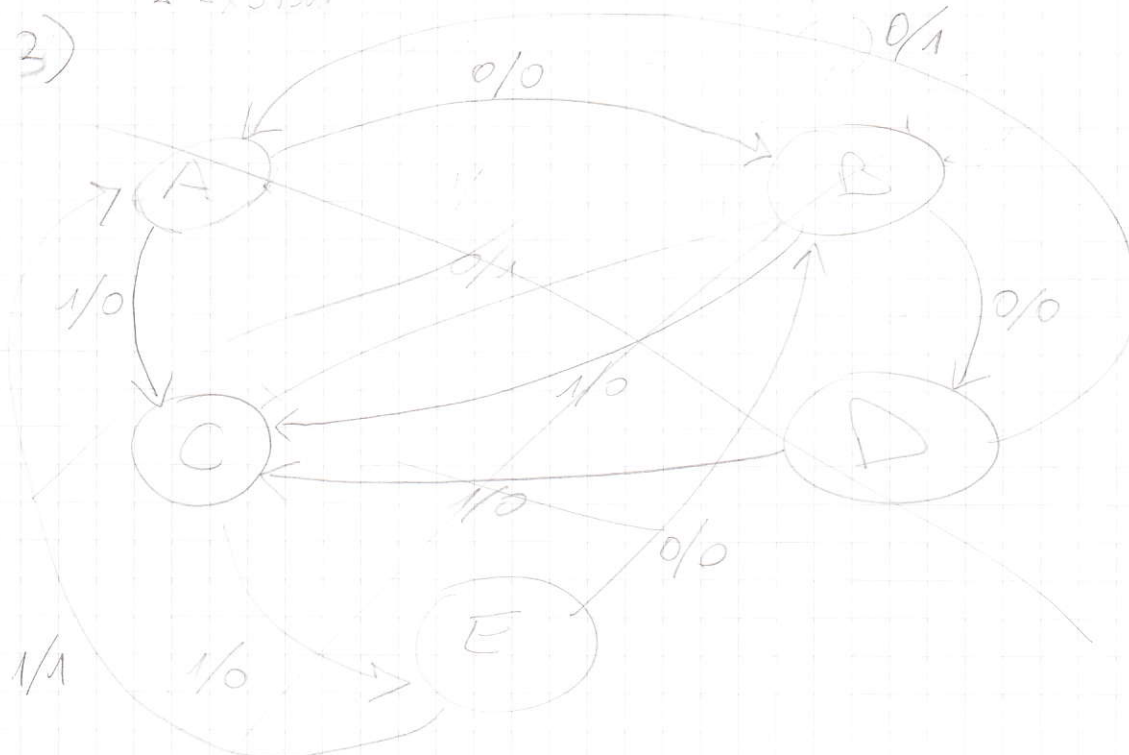

26. gem 05

2) Integri a NAND

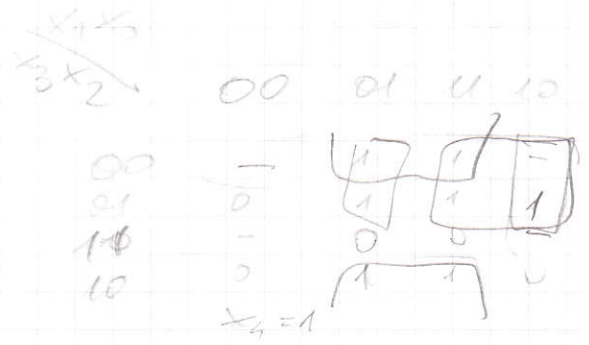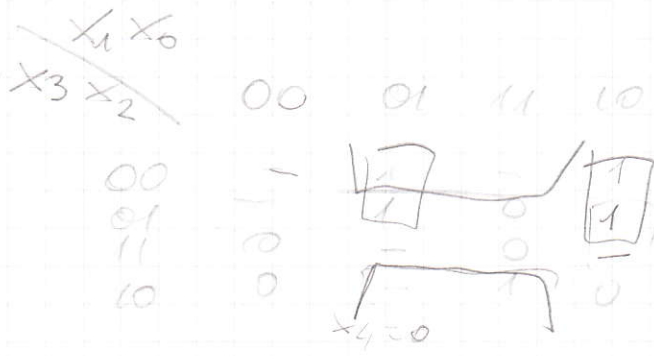

$$x_0 \overline{x_2} + \overline{x_0} x_1 \overline{x_3} + x_0 \overline{x_1} \overline{x_3} + x_1 \overline{x_3} x_4$$

$$= \overline{x_0} \overline{x_2} \cdot \overline{x_0} x_1 \overline{x_3} \cdot x_0 \overline{x_1} \overline{x_3} \cdot x_1 \overline{x_3} x_4$$

