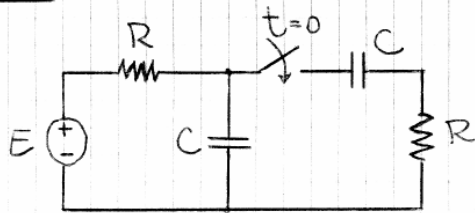


ES. 1


16/02/06



$$R = 1 \Omega$$

$$C = 1 \mu F$$

circuito trasformato:

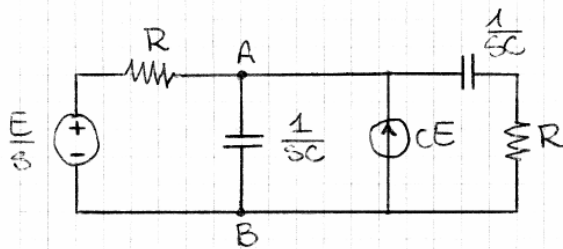

$$V_{AB} = \frac{\frac{E}{sR} + CE}{\frac{1}{R} + Cs + \frac{1}{R + 1/sC}} = \frac{1}{s} \cdot \frac{\frac{E}{R} + CSE}{\frac{1 + CSR}{R} + Cs(SCR + 1) + Cs} =$$

$$= \frac{E}{sR} \cdot \frac{(1 + RCS) \cdot (1 + RCS)}{\frac{1}{R} (1 + CSR + C^2 s^2 R^2 + CSR + CSR)}$$

$$= \frac{E}{s} \cdot \frac{(1 + CSR)^2}{C^2 s^2 R^2 + 3CSR + 1} = \frac{E}{sC^2 R^2} \cdot \frac{(1 + CSR)^2}{s^2 + 3 \frac{s}{CR} + \frac{1}{C^2 R^2}}$$

$$s^2 + 3 \frac{s}{CR} + \frac{1}{C^2 R^2} = 0$$

$$s_{1,2} = -\frac{1}{CR} \cdot \left( \frac{3 \pm \sqrt{5}}{2} \right)$$

$$V_{AB} = \frac{10^6 E}{s} \cdot \frac{(1 + 10^{-3} s)^2}{\left( s + 10^3 \cdot \frac{3 + \sqrt{5}}{2} \right) \cdot \left( s + 10^3 \cdot \frac{3 - \sqrt{5}}{2} \right)}$$

$$V_{AB} = 10^6 E \cdot \left[ \frac{A}{s} + \frac{B}{s + 10^3 \cdot \frac{3 + \sqrt{5}}{2}} + \frac{C}{s + 10^3 \cdot \frac{3 - \sqrt{5}}{2}} \right]$$


$$A = \frac{1}{10^3 \cdot \frac{3 + \sqrt{5}}{2} \cdot 10^3 \cdot \frac{3 - \sqrt{5}}{2}} = 10^{-6} \cdot \frac{9 - 5}{4} = 10^{-6}$$

$$B = \dots = \frac{10^{-6}}{\sqrt{5}} \quad ; \quad C = -\frac{10^{-6}}{\sqrt{5}}$$

$$v_{AB}(t) = E \cdot \left[ 1 + \frac{1}{\sqrt{5}} e^{-10^3 \frac{3 + \sqrt{5}}{2} t} - \frac{1}{\sqrt{5}} e^{-10^3 \frac{3 - \sqrt{5}}{2} t} \right]$$

Es. 2

16/02/06

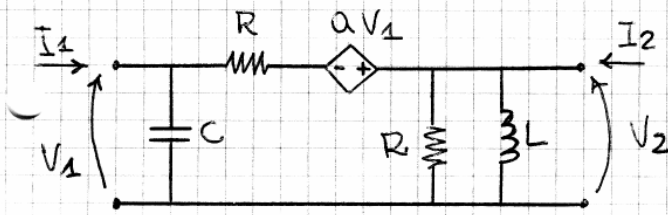

$$R = 0.5 \Omega$$

$$a = k+1$$

$$L = 0.5 \text{ H}$$

$$C = 1 \text{ mF}$$

$$\begin{cases} I_1 = Y_{11} V_1 + Y_{12} V_2 \\ I_2 = Y_{21} V_1 + Y_{22} V_2 \end{cases}$$


$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

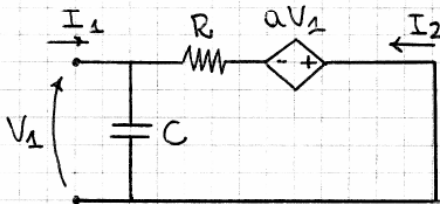$Y_{11}$  e  $Y_{21}$  si calcolano cortocircuitando la porta 2




$$I_1 = SCV_1 + \frac{aV_1 + V_1}{R}$$

$$Y_{11} = SC + \frac{a+1}{R} = SC + \frac{k+2}{R}$$

$$I_2 = \frac{-aV_1 - V_1}{R}$$

$$Y_{21} = \frac{-aV_1 - V_1}{V_1 R} = \frac{-a-1}{R} = \frac{-k-2}{R}$$

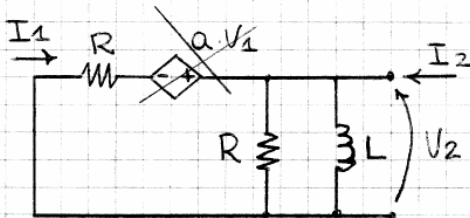$Y_{12}$  e  $Y_{22}$  si calcolano cortocircuitando la porta 1




$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{1}{2R} + \frac{1}{sL}$$

$$I_1 = -\frac{V_2}{R}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = -\frac{\frac{V_2}{R}}{V_2} = -\frac{1}{R}$$
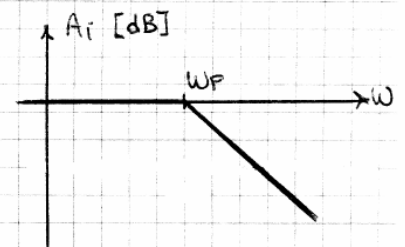
$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} SC + \frac{k+2}{R} & -\frac{1}{R} \\ \frac{-k-2}{R} & \frac{1}{2R} + \frac{1}{sL} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$



$$A_i = \frac{I_2}{I_1} \Big|_{V_2=0} = \frac{\frac{-aV_1 - V_1}{R}}{SCV_1 + \frac{aV_1 + V_1}{R}} = \frac{-(a+1)}{SCR + a+1} = -\frac{a+1}{SCR + a+1}$$

$$A_i = -\frac{1}{S \frac{CR}{a+1} + 1}$$